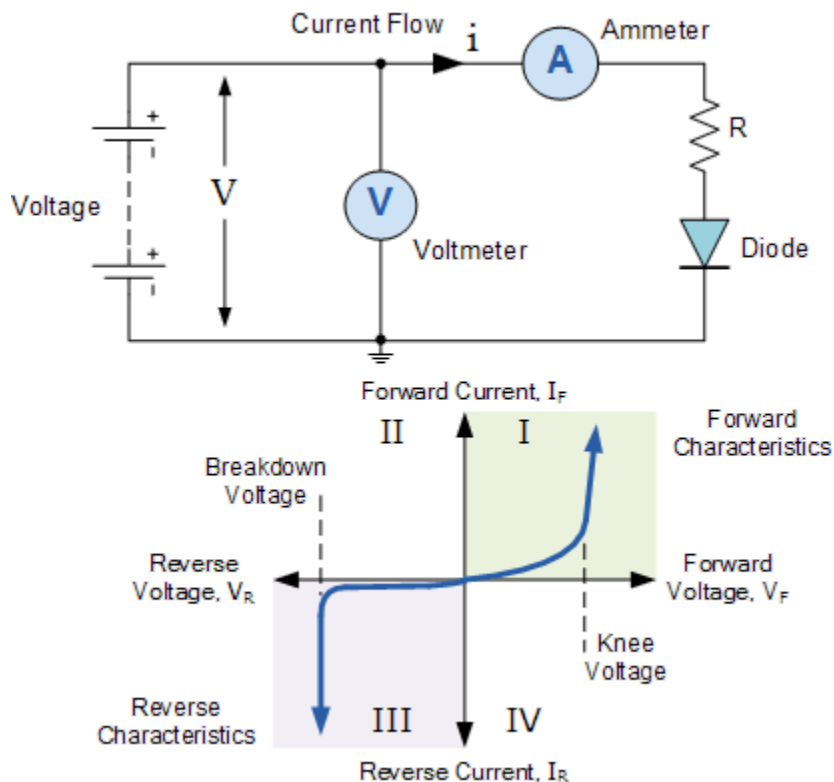


Basics


- Signal generator
- Oscilloscope
- Breadboard connection and power supply
- Load resistor.

How do you implement following experiment :


1. I-V characteristics of diode
IC : 1N4007



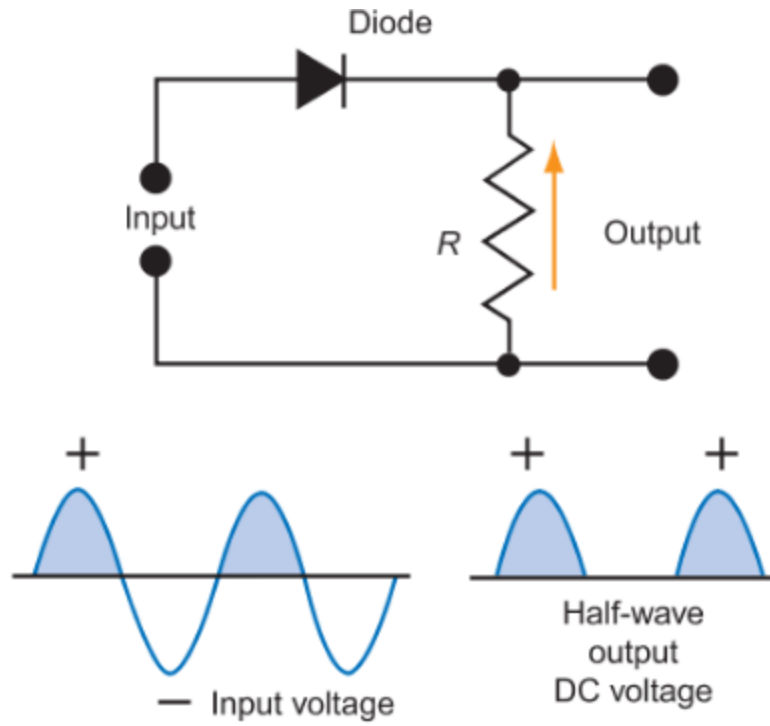
- a. Voltage source
 - b. Multimeter
 - c. Diode 1N4007
 - d. Load resistance (1k-100k Ohm)
2. Half-wave rectification



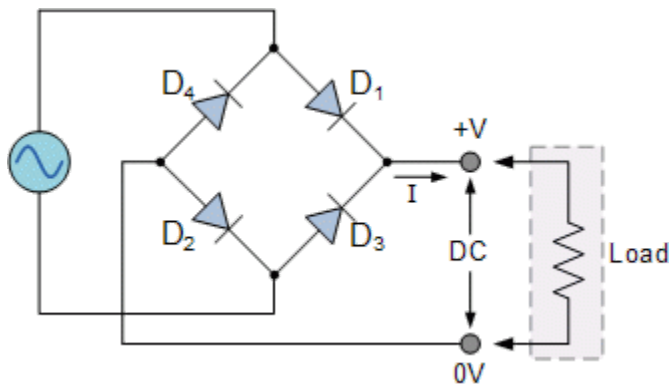- a. Signal generator
 - b. Oscilloscope
 - c. Diode 1N4007
 - d. Load resistance
3. Full wave rectification



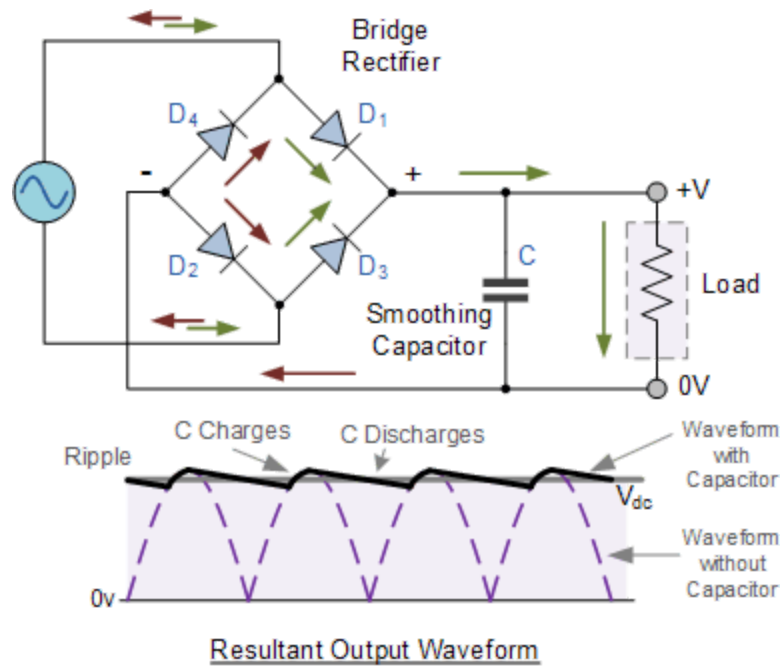- a. Signal generator
- b. Oscilloscope
- c. Diode 1N4007
- d. Load resistance



- e. Capacitor
4. Transistor characteristics (common base/emitter)
 - a. Voltage source
 - b. Multimeter
 - c. BJT 2N3904, 2N3906, 2N2222,
 - d. Load resistance (1k-100k Ohm)
5. Op Amp 741 IC